 


Peripheral Interface Device (8255 modes and examples)

Dr A Sahu
Dept of Computer Science & Engineering
IIT Guwahati

Hierarchy of I/O Control Devices




Outline

- 8255 Architecture and its block diagram
- 8255 Ports and mode of operations
- BSR Mode
- Mode 0
 - Interfacing A/D Converter using Handshake mode using 8255
- Mode 1
 - Interfacing DIP keyboard using Handshake mode using 8255
- Mode 2
 - Interfacing keyboard (with bounce) using Handshake mode using 8255
- Introduction to interrupt controller (8259A)


Block Diagram of 8255

CS ^b	A1	A0	Sel
0	0	0	Port A
0	0	1	Port B
0	1	0	Port C
0	1	1	CRW


Bi directional
Data Bus
D7-D0

 


Ports & Modes in 8255

 

Ports & Modes in 8255 : Control register

 


I/O port Addressing

 

CS ^b	A1	A0	HEX Address	Port
A7 A6 A5 A4 A3 A2	A1	A0		
1 0 0 0 0 0	0	0	= 80H	A
	0	1	=81H	B
	1	0	=82H	C
	1	1	=83H	Control Register

Ports

 - Control register controls the overall operation of 8255
- All three ports A, B and C are grouped into two



Operation modes

- 8255 has three modes:
 - Mode 0: basic input-output
 - Mode 1: Strobbled input-output
 - Mode 2: Strobbled bi-directinal bus I/O
- In mode 0
 - Two 8-bit ports and two 4-bit ports
 - Any port can be input or output
 - Outputs are latched, inputs are not latched

Operation modes

- In mode 1:
 - Three ports are divided into two groups
 - Each group contains one 8-bit port and one 4-bit control/data port
 - 8-bit port can be either input or output and both latched
 - 4-bit port used for control and status of 8-bit data port
- In mode 2
 - Only port A is used
 - Port A becomes an 8-bit bidirectional bus
 - Port C acts as control port (only pins PC3-PC7 are used)

BSR (Bit Set or Reset Mode)

- Set/Reset bit of Port C
- Heavily used for HS and Interrupt mode
- BSR Control word

D7	D6	D5	D4	D3	D2	D1	D0
0 BSR Mode	Not used, So (000)			Bit Select			S/R (1/0)

- BSR Control word
 - To set PC7= 0 000 111 1 (0FH)
 - To reset PC7= 0 000 111 0 (0EH)
 - To set PC3 = 0 000 011 1 (07H)

BSR Mode example

- BSR Control word
 - To set PC7= 0 000 111 1 (0FH)
 - To reset PC7= 0 000 111 0 (0EH)
 - To set PC3 = 0 000 011 1 (07H)

D7	D6	D5	D4	D3	D2	D1	D0
0 BSR Mode	Not used, So (000)			Bit Select			S/R (1/0)

Generate Activation pulse of Delay D on PC7&PC3

```
MVI    A,0FH        ; Load ACC to set PC7
OUT     83H          ; set PC7=1
MVI     A,07H        ; Load ACC to set PC3
OUT     83H          ; set PC3=1
CALL    DELAYD;
MVI     A,06H        ; Load ACC to Reset PC3
OUT     83H          ; set PC3=1
MVI     A,0EH        ; Load ACC to Reset PC7
OUT     83H          ; set PC7=1
```

8255: Mode 0

- Simple I/O for port A,B,C
- Output are latched
- Input are not latched
- Port don't have HS or interrupt capability


8255: Mode 0, Example 1

- Configure
 - Port A and port C_U as out port
 - Port B and port C_L as in port
- Interface to Read from I/P DIPs and Display at O/P LEDs
- Control word

D7	D6	D5	D4	D3	D2	D1	D0
1	0	0	0	0	0	1	1
I/O function	Port A in Mode 0		Port A as O/P	Port C_U As O/P	Port B in Mode 0	Port B As I/P	Port C_L As I/P

83H

Interface Circuit

 

Interface Program

```
MVI  A,83H    ; Load acc with Control word
OUT  83H      ; Load control register with 83
             at port address 83
IN81H        ; Read DIP from port B
OUT  80H      ; Write to LEDs
IN 82H       ; Read DIP from port C
ANI  0FH      ; Mask upper part of
             port C are not i/p
RLC RLC RLC RLC; Rotate 4 time
OUT  82H      ; Display data at port CU
HLT
```


8255: Mode 0, Example 2

- Air Conditioning Room (Temperature Control)
 - Heater and Cooler
 - Temperature Sensor
 - A/D converter
 - Driver Switch to drive Heater/Cooler
- Design an A/C controller using 8255 and 8085 based interfacing circuit
- Read temperature and control the temperature between 20-30 degree Celcius

8255: Mode 0, Example 2

- Air Conditioning Room (Temperature Control)
 - Heater and Cooler
 - Temperature Sensor
 - A/D converter
 - Driver Switch to drive Heater/Cooler
- Design an A/C controller using 8255 and 8085 based interfacing circuit
- Read temperature and control the temperature between 20-30 degree Celsius
- **Use port A in mode 0 and Port C in BSR mode**

Interface Circuit

 

Interface control

- Control word

- Port A as I/P from ADC
- Port C_L : as I/P PC_0 is used for end of conversion
- Port C_U : as O/P PC_4 -> Start con. PC_7 -> assert RD^b signal

D7	D6	D5	D4	D3	D2	D1	D0
1	0	0	1	0	0	0	1
I/O function	Port A in Mode 0		Port A as I/P	Port C_U As O/P	Port B Is Not used		Port C_L As I/P

91H

- BSR Control word

- 0 (mode) 000 (don't care) 000 (0/1=set/reset)
- Set PC_7 high = 0 000 111 1 = 0FH (Send RD^b to ADC)
- Set PC_4 low = 0 000 100 0 = 08F (send Start Conv WR^b)
- Set PC_5 high = 0 000 101 1 = 0BF (Fan On)
- Set PC_5 low = 0 000 101 0 = 0AF (Fan Off)

Interface Program to do Temp. Control

```
MVI A, 91H ; mode 0 control word
OUT 83H ; Set A& CL as I/P & CU as
        O/P
```

```
MVI A, 0FH ; Set PC7 High
OUT 83H ; Disable RDb
MVI A, 08H ; Set PC4 WRb low
OUT 83H ; Start conversion
MVI A, 09H ; Set PC4 WRb high
OUT 83H ; Ser WRb high
```

```
RD: IN 82H ; Read Port C to Chck PC0
    RAR ; Place PC0 in Carry Flag
    JC RD ;if PC0=1, read Again
    MVI A, 0EH ; Set PC7 RDb low
    OUT 83H ; Assert RDb signal
    IN 80H ; Read A/D conv. Port A
    MOV B, A ; get temp in B
```

```
MVI A 0FH; ; Set PC7 (RDb) high
OUT 83 ; Disable RDb
MOV A,B;
CPI 30D;
CNC COOLEROFF; PC5 off 0AH
CC COOLERON; PC5 on 0BH
CPI 10D;
MOV A,B;
CNC HEATERON; PC6on: 0CH
CC HEATEROFF; PC6off: 0DH
RET
```

```
COOLEROFF:
    MVI A, 0AH ; Reset PC5 to turn off Cooler
    OUT 83H
    RET
```

8255: Mode 1

- Two port A & V function 8 bit I/O
 - Configured either Input or output port
- Each port each 3 lines of port C as HS signal
 - Remaining two lines can be used as simple I/O
- Input and output are latched
- Interrupt logic is supported

PC6, PC7 in
In/Out mode

D7	D6	D5	D4	D3	D2	D1	D0
1	0	1	0	0/1	1	1	X=0
I/O function	Port A in Mode 1		Port A as O/P	Port C _U As O/P	Port B in Mode 1	Port B As I/P	Port C _L As I/P

AEH

8255: Mode 1: Input Control signal

- STB^b: Strobe generated by Peripheral
- IBF: Input buffer full
 - Acknowledge by 8255 to I/O that I/O latched received
 - Reset when MPU read the data
- INTR: output signal to MPU and it generate when STB^b=1, IBF=1 and INTE=1
- INTE: Enable or disable Interrupt
 - INTE_A is through PC₄, INTE_B is through PC₂
- Status word

D7	D6	D5	D4	D3	D2	D1	D0
OBFB _A	INTE _A	1/0	1/0	INTR _A	INTE _B	OBFB _B	INTR _B

Mask with 02H

8255: Mode 1, Example


- Designing for interfacing
 - Keyboard with interrupt I/O in port A
 - Output port for a printer using status check I/O
- Control word

D7	D6	D5	D4	D3	D2	D1	D0
1	0	1	1	0	1	0	0
I/O function	Port A in Mode 1		Port A as I/P	PC _{6,7} as X	Port B in Mode 1	Port B As O/P	Don't care

B4H

- To generate interrupt $INTE_A$ PC₄ to set in BSR mode
 - 0 (mode) 000 (don't care) 000 (0/1=set/reset)
 - Set PC4 High = 0 000 100 1 = 09F (send INTR to MPU RST 6.5)

Interface Circuit

 

Interface Program

Initialization Program

MVI A, B4H ; initialize port A as IP and B as O/P

OUT 83H

MVI A,09H ; Set INTEA , that is PC4

```

EI          ;Enable interrupt

```

CALL PRINT ; Continue other Task

ISR at 0034 at RST6.5 vector location

```
0034:  JMP  READPORTA
```

READ PORTA:

DI

IN 80H

MOV M, A

INX H

EI

RET

```
PRINT:  LXI H MEM
```

MVI B COUNT

MOV A,M

MOV C,A

STATUS: IN 82H ; from port C for
Status OBF^b

ANI 02H

JNZ STATUS

MOV A,C

OUT 81H; Send to port B
printer

INX H

DCR B

JNZ NEXT


RET

8255: Mode 2: Bi-directional Data transfer

- Bi-directional
 - Data transfer between two MPU
 - Data transfer between MPU and Controller
- **Port A can be bi-directional, Port B in either 0 or 1 mode**
- **Port A use 5 signals from port C as Handshake signal for data transfer**

Bi-directional Data transfer between two MPU

 - One is Master other is Slave
- Use 8255 as Interfacing device




Data Transfer From Master to Slave

- Master read the status of OBF to verify whether the previous byte has read by Slave
- Master **write data in port A** and 8255 inform to Slave by OBF^b low
- Slave check OBF for data availability
- Slave **read the data from port A** and ACK low to 8255

Data Transfer From Slave to master

- Slave check the HS signal IBF to find out whether port A is available or not
- Slave **Write a data in port A** and inform 8255 by enabling STB^b low
- 8255 causes a IBF to go high and MPU get the signal the data byte to read
- Master **read the data from port A** and make IBF low

Interface Circuit

 

Control word Mode 2

- Control word

D7	D6	D5	D4	D3	D2	D1	D0
1	1	X	X	X	1/0	1/0	1/0
I/O function	Port A in Mode 1		Port A as Bi		Port B in Mode 1/0	Port B As 1/0	Port C

C0H

Port C bit 2,1,0
mode 0/1

- Status word:

D7	D6	D5	D4	D3	D2	D1	D0
OBF _A	INTE ₁	IBF _A	INTE ₂	INTR _A	X	X	X

**RAL instruction to get
the Status**

Interface program: Master & Slaves

Master:

```
LXI H, MemptrM
MVI B, Byte2Trasfer
MVI A, CTRL; Control word for
Mode 2
OUT 83H; Write Control word
```

OBFLO:

```
IN 82H ; Read port C
RAL ; place OBF in CY
JNC OBFLO;
```

```
OUT 80H ; place on Port A
INX H
DCR B
JNZ OBFLO
```

```
HLT
```

SLAVE:

```
LXI H, MemptrS
MVI B, Byte2Trasfer
```

OBFHI:

```
IN 87H ; Read port C
RAL ; place OBF in CY
JC OBFHI;
```

```
IN 85H ; Read from Port A
MOV M, A
```

```
INX H
DCR B
JNZ OBFHI
HLT
```

Introduction to Interrupt controller

8259A

- Acts as a multiplexer, combining multiple interrupt input sources into a single interrupt output to interrupt a single device.
- Original PC introduced in 1981
- Eight interrupt input request lines
 - IRQ0 - IRQ7,
 - An interrupt request output line named INTR
 - Interrupt acknowledgment line named INTA
 - D0 through D7 for communicating the interrupt level or vector offset.
- There are three registers
 - Interrupt Mask Register (IMR)
 - Interrupt Request Register (IRR)
 - In-Service Register (ISR)

Reference

- R S Gaonkar, “Microprocessor Architecture”, Chapter 15

Thanks