


$$R = \frac{E_i - E_o}{I_z + I_{L \max}}$$

chapter-1

Ex-1.1


Maximum power transfer theorem

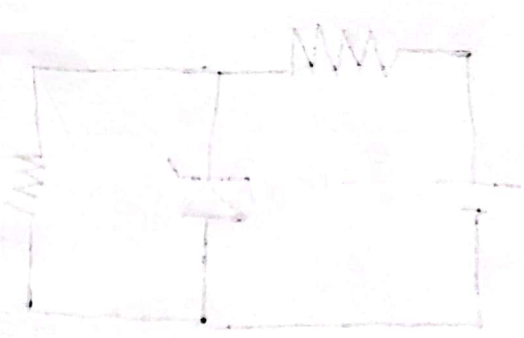Maximum power is transferred from a source to a load when the load resistance is made equal to the internal resistance of source



$$I = \frac{V_{th}}{R_{th} + R_L}$$
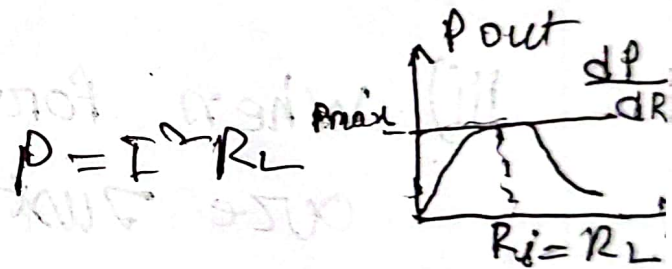
$$P = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$



$$\frac{dP}{dR_L} = 0$$

$$\Rightarrow \frac{d}{dR_L} \left(\frac{V_{th}^2}{(R_{th} + R_L)^2} \times R_L \right) = 0 \Rightarrow V_{th}^2 \frac{d}{dR_L} \left(\frac{R_L}{(R_{th} + R_L)^2} \right)$$

$$\Rightarrow V_{th}^2 \left[\frac{(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)}{(R_{th} + R_L)^4} \right] = 0$$

$$(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L) = 0$$

$$\Rightarrow (R_{th} + R_L)^2 = 2R_L(R_{th} + R_L)$$

$$\Rightarrow R_{th} + R_L = 2R_L$$

$$\Rightarrow R_{th} = R_L$$

Load resistance = internal resistance

Ex-1.5

Questionsolve 20-21

1a) The electrons in the outermost orbit of an atom are known as valence electrons.

On the basis of electron conductivity material are generally classified into conductor, insulator, and semiconductors.

Conductor

When the number of valence electrons is less than 4, the material is usually a metal and a conductor.

Ex: Sodium, Magnesium.

Insulator

When the number of valence electrons of an atom is more than 4, the material is usually a non-metal and an insulator.

Ex. Nitrogen, Sulphur.

Semiconductor

When the number of valence electrons of an atom is 4, the material has both metal

TOPIC NAME : _____

DAY : _____

TIME : _____ DATE : / /

and non-metal properties and is usually a semiconductor. Examples are carbon, silicon, germanium

~~b) A direct voltage source is a device that provides~~

b) There are two types of voltage source

i) Direct voltage source

ii) Alternative voltage source

i) Direct Voltage source


A direct voltage source provides a constant voltage output with a fixed polarity meaning the positive and negative terminals remain fixed. Ex

Example: battery cells, dc generators.

When a load resistance is connected a direct current flows from the positive terminal to the negative terminal through the load.

GOOD LUCK™

Figure

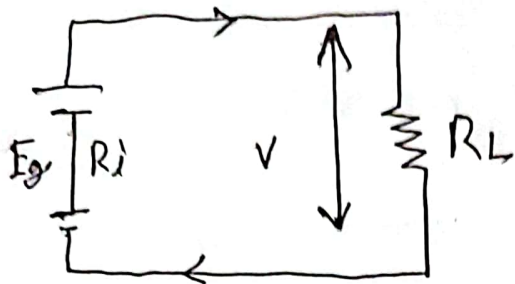

equation

Load current, $I = \frac{E_g}{R_L + R_i}$

Terminal voltage $V = E_g - IR_i$ or IR_L


ii) Alternating ~~current~~ voltage source

A device which produces alternating voltage output continuously is known as alternating voltage source.

Ex. ac generator.

An important characteristic of alternating voltage source is that it periodically reverses the polarity of the output voltage.

Figure:

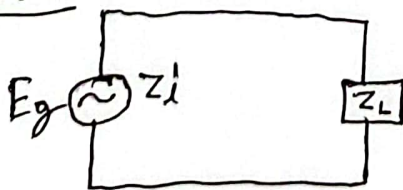

equation:

Load current $I (r.m.s) = \frac{E_g}{Z_i + Z_L}$

Terminal voltage, $V = (E_g - IZ_i)$
or IZ_L

book ex-1.1

c) $E_0 = 24 \text{ V}$
 $r_i = 0.01 \Omega$
 Power = 100 watt

$P = E_0 \times I$

$I = \frac{100}{24} = 4.17 \text{ A}$



(i) voltage drop internal resistance = 4.17×0.01
 ~~$= 0.0417 \text{ V}$~~
 $= 0.0417 \text{ V}$

(ii) Terminal voltage drop = $24 - 0.0417 \text{ V}$
 $= 23.96 \text{ V}$

A device which produces electromotive force (EMF) is known as an electromotive force source. The EMF of a source is the potential difference between the terminals of the source when no current is drawn from it. In other words, it is the open circuit potential difference across the terminals of the source.

Terminal voltage (V) is the potential difference across the terminals of the source when current is drawn from it. It is less than the EMF of the source.

