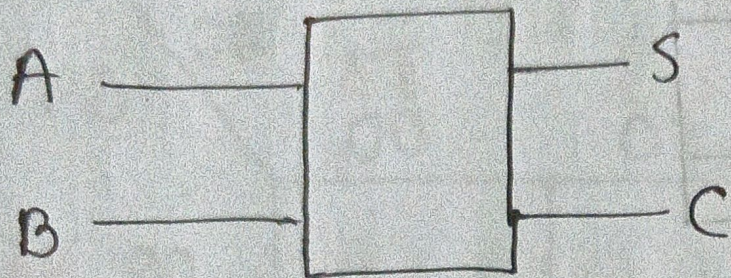


Adder

* Half - Adder


↳ use to add two 1 bit binary digit




A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$

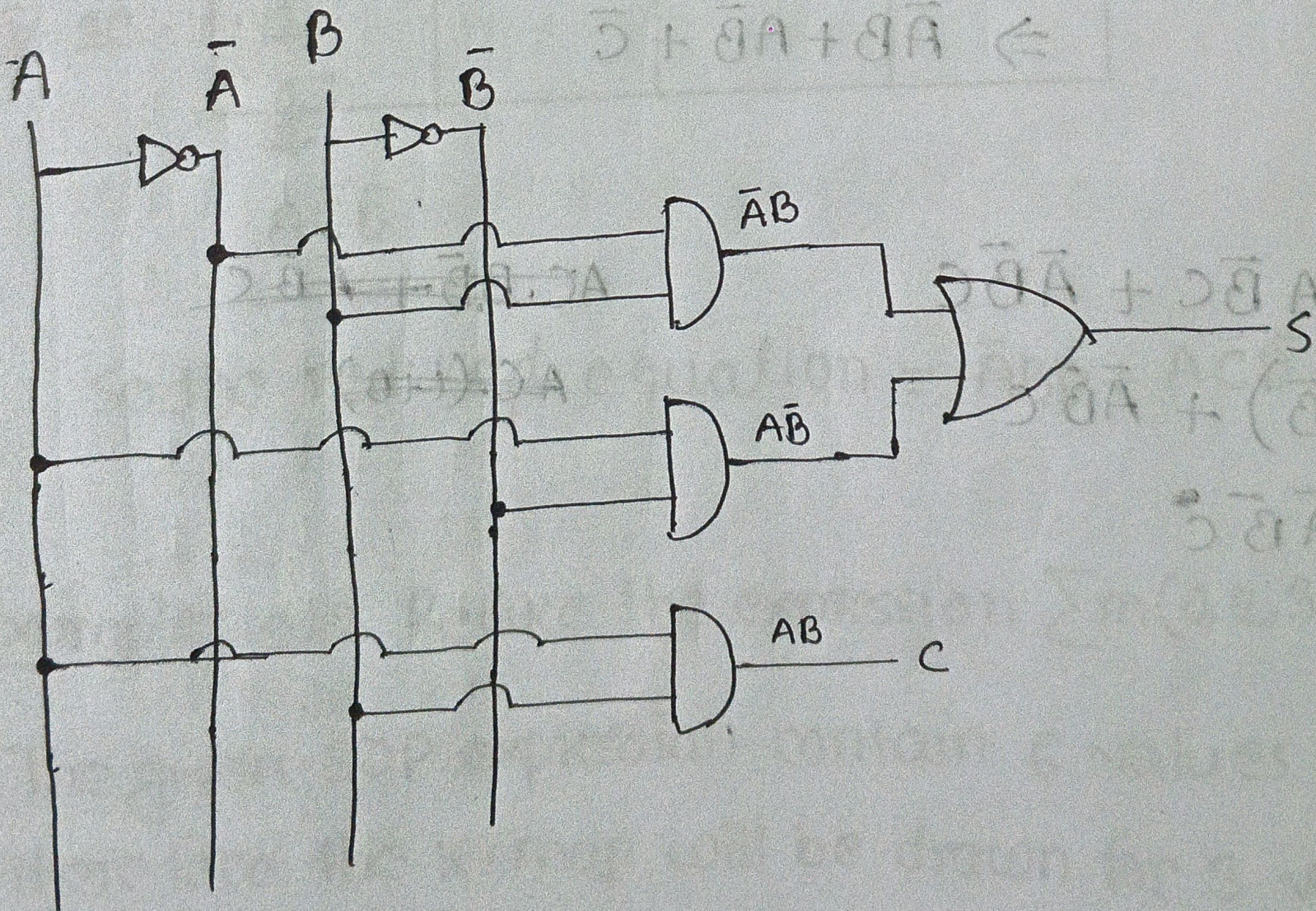

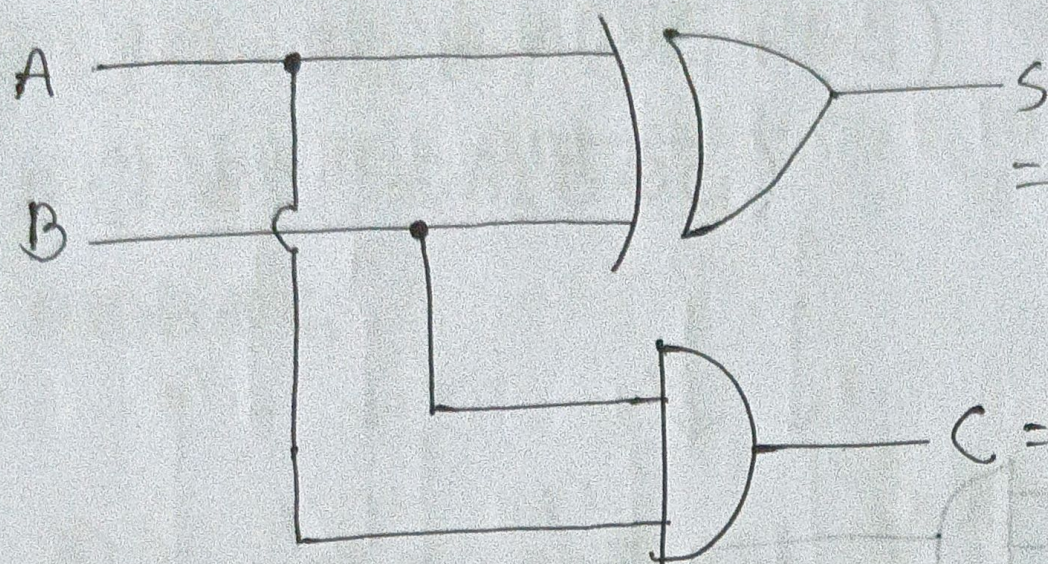

$$= A \oplus B$$


$$C = A \cdot B$$

(distributive law)

$$C + \bar{C}A = (C + A)$$

* Full adder

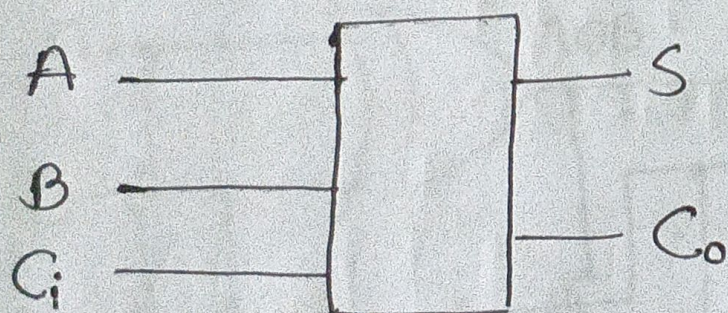A full adder is a digital circuit that adds three binary numbers and produces the sum and carry.



A	B	C _i	S	C _o
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + ABC_i + ABC_i$$

$$= \bar{A}BC_i + A\bar{B}C_i + AB(\bar{C}_i + C_i)$$

$$= \bar{A}BC_i + A\bar{B}C_i + AB$$

$$= \bar{A}BC_i + A(\bar{B}C_i + B)$$


$$= \bar{A}BC_i + A(B + C_i)$$

$$= \bar{A}BC_i + AB + AC_i$$

$$= C_i(\bar{A}B + A) + AB$$

$$= C_i(A+B) + AB$$

$$= AC_i + BC_i + AB$$

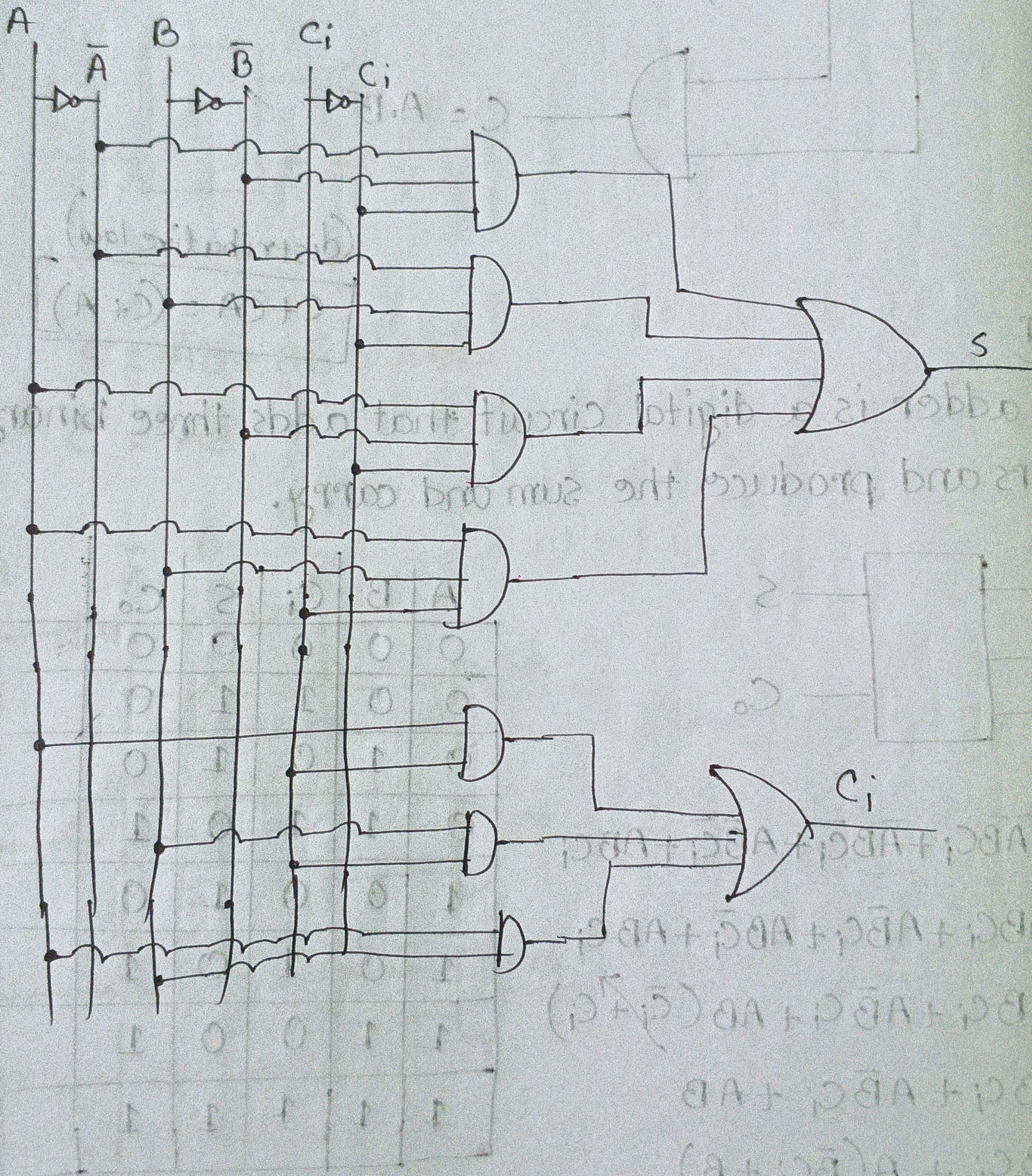

$$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$$

$$= \bar{A}(\bar{B}C_i + B\bar{C}_i) + A(\bar{B}\bar{C}_i + BC_i)$$

$$= \bar{A}(B \oplus C_i) + A(\overline{B \oplus C_i})$$

$$= A \oplus B \oplus C_i$$


$$C_o = \bar{A}BC_i + A\bar{B}C_i + ABC_i + ABC_i$$

$$= \bar{B}(\bar{A}C_i + AC_i) + AB$$

$$= \bar{B}C_i(\bar{A} + A) + AB$$


$$= C_i(\bar{A}B + A\bar{B}) + AB$$

$$= C_i(A \oplus B) + AB$$

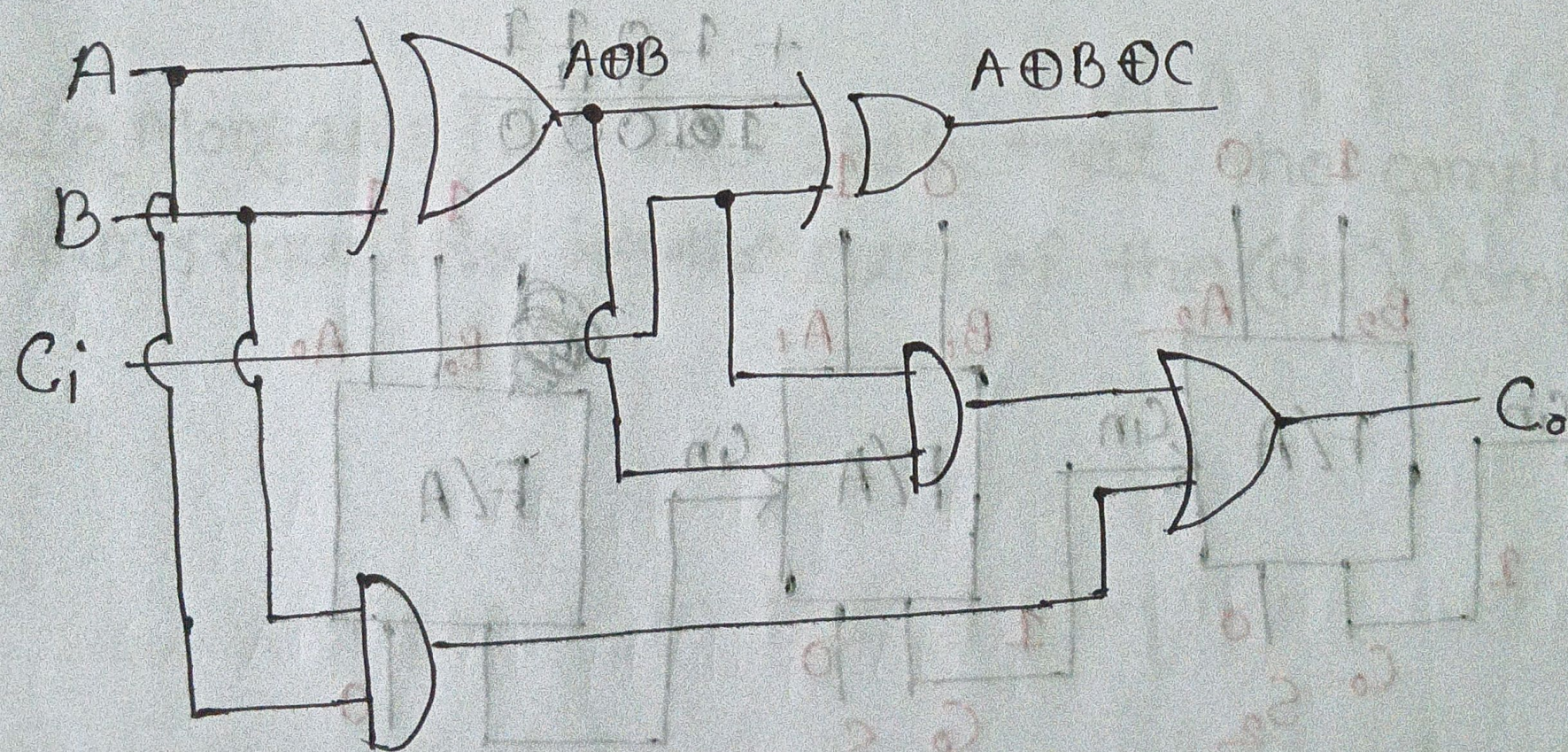

4-bit adder

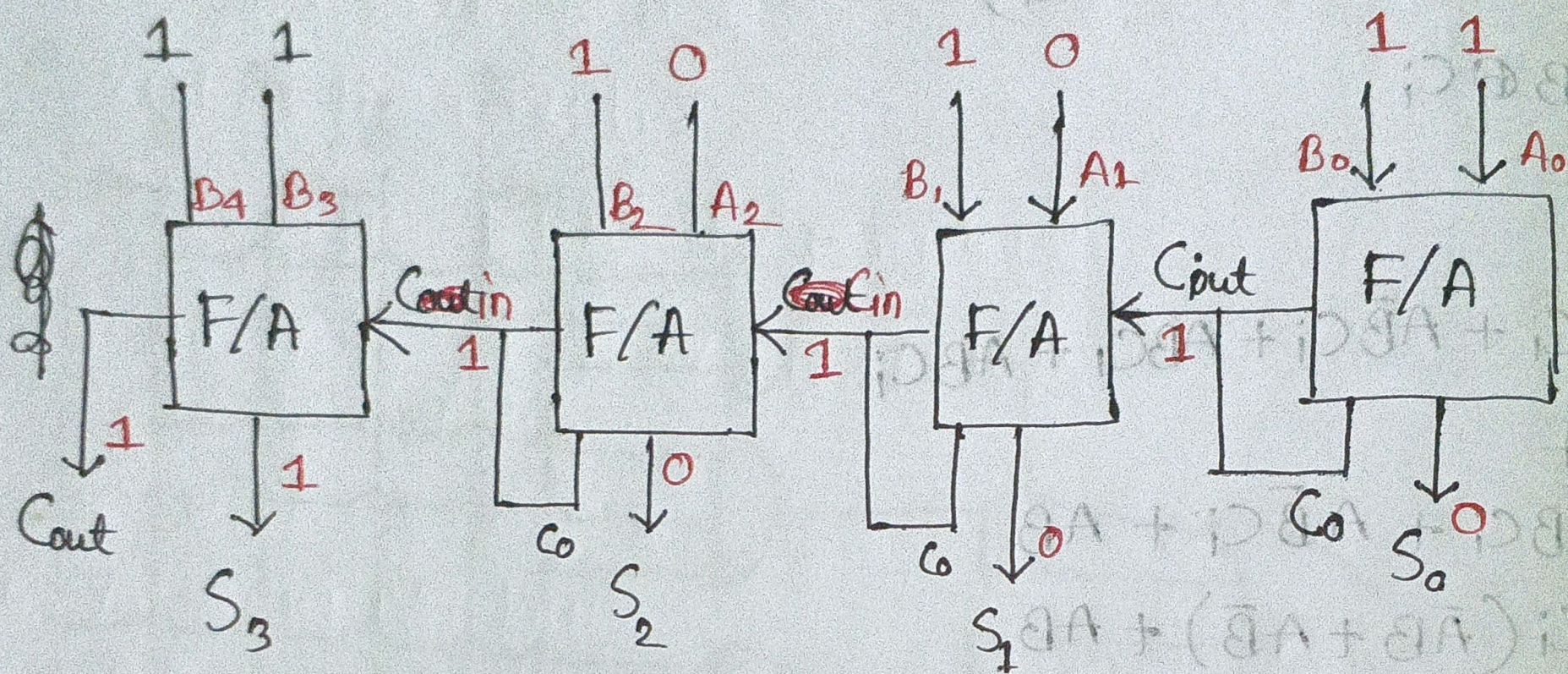A 4-bit adder is a digital circuit that helps the CPU in performing addition of two 4-bit binary numbers.



$$\begin{array}{r}
 1101 \\
 + 1011 \\
 \hline
 101000
 \end{array}$$

