

Experiment: 2

Title: V-I characteristics of p-n junction diode.

Aim: To plot the V-I characteristics of p-n junction diode in forward and reversed bias and also to calculate static and dynamic resistance.

Apparatus:

i) 1N4007 diode ii) Resistor $1\text{ K}\Omega, 470\Omega$ iii) Ammeter
iv) Voltmeter v) TRPS vi) BreadBoard vii) Wires.

Circuit Diagram:

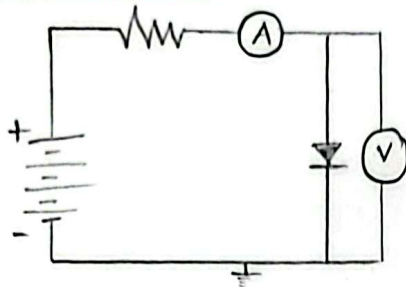


fig: Forward bias

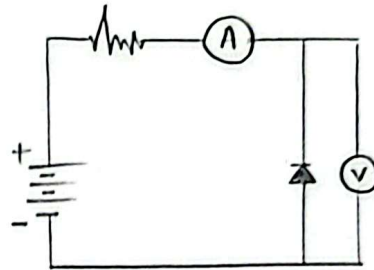



fig: Reverse bias

Table:

V_f	$I_f (\text{mA})$
0	0
0.30	0
0.46	0.1

V_r	$I_r (\mu\text{A})$
0	0
0.14	12.4 μA
0.20	26.1 μA

Graph:

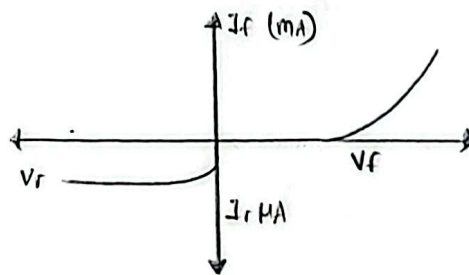

Procedure:

• Forward bias:

- Make connection according to circuit diagram.
- In forward connect positive to anode and negative to cathode.
- By varying Voltage take reading
- Plot the graph between forward and reversed bias.

Reverse Bias:

- Make connection According to circuit diagram.
- Connect positive to cathode and negative to anode.
- By Varying Voltage take the reading.

Calculation:

- Static resistance = V/I at a-point.
- Dynamic Resistance = $\Delta V / \Delta I$ at Q-point.

Precautions:

- Connection must be made carefully to avoid short circuit.

Result:

the VI characteristics of p-n junction are observed and the graph are plotted.

Static resistance = 4.6

Dynamic resistance = 4.6

Cut-in voltage = 0.46 V

Experiment-3:

Title: VI characteristics of Zener diode and zener diode regulator.

Aim: To plot the VI characteristics of Zener diode in reverse and to verify that Zener diode acts as a voltage regulator.

Apparatus:

- i) Zener Diode ii) 470 Ω resistor iii) Ammeter
iv) Voltmeter v) TRPS vi) Breadboard vii) Wire.

Circuit Diagram:

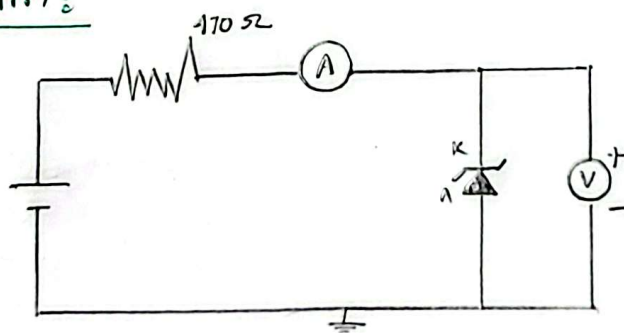



fig: Reverse bias

Procedure:


(a) To plot V_I characteristics:

- Make the connection as per diagram.
- Vary the RPS Voltage from 0V to 30V in steps of 4V.
- Tabulate the reading of Ammeter and voltmeter.
- Plot the graph between V_Z and I_Z
- Calculate the breakdown voltage of given Zener diode from the graph.

Model graph:

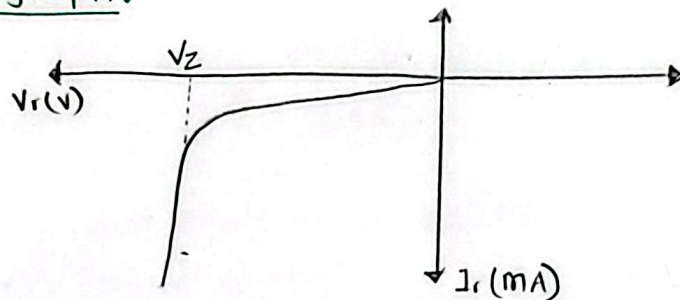

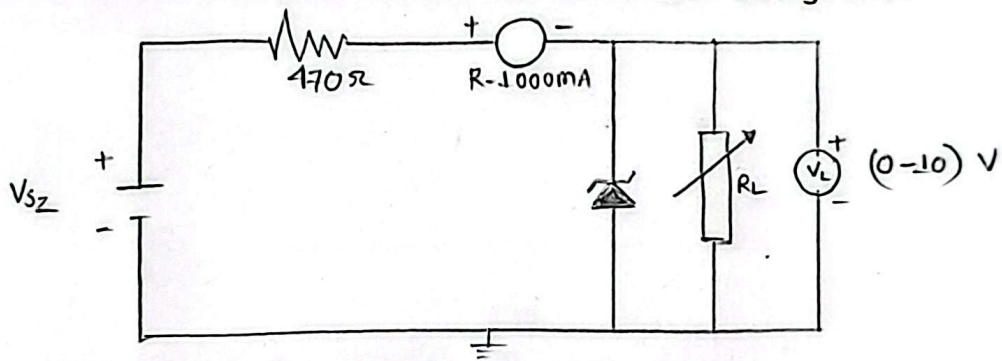Circuit Diagram: Zener diode as Voltage Diagram.



Tabular form:

S No	R_L (ohm)	V_Z (Volts)	$I_S = I_Z + I_L$	% regulation ($(V_{NL} - V_L) / V_L \times 100$)
	1100Ω			
	to			
	100Ω			

Procedure:

(b) As voltage regulator:

- Make the connection as shown in the figure.
- Measure V_{NL} (No load voltage) and vary the load resistance from 100Ω to 1100Ω.
- Tabulate the data and calculate.

Precautions:

- Connection must be made carefully to avoid short circuit
- Reading must be taken without parallax error.

Result:

- The reverse bias characteristics are observed.
- The regulation characteristics are also plotted.

Experiment: 4:


• Title: VI characteristics of Light emitting diode (LED)

• Aim: To determine the forward bias characteristics of the light emitting diode (LED).

Apparatus:

- i) LED ii) 470Ω resistance iii) Voltmeter iv) Ammeter
v) TRPS vi) Bread board.

Circuit Diagram:

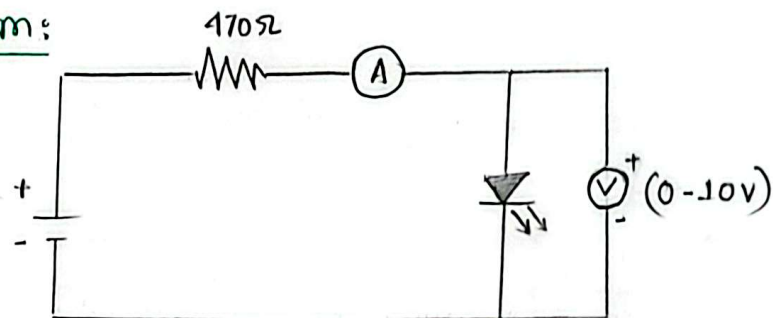


Procedure:

- Connection must be made as per circuit diagram.
- By Varying voltage in steps note down current.
- At the same time note the intensity.

Table:

SL NO	V_f Voltage	I_f (mA)	Intensity
01	1	0	Dim
02	2	0	Dim
03	2.4	0.5	Low-mid
04	2.8	6	mid
05	2.9	10	high

• Model graph:

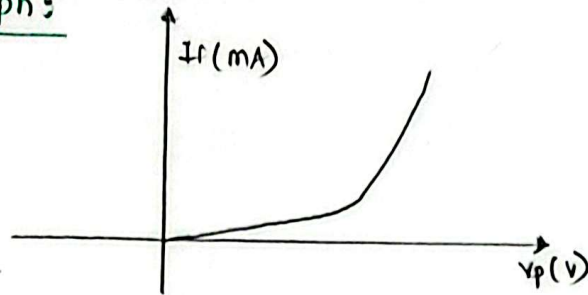

• Precautions:

- Connection must be followed carefully
- Reading should not exceed meter range.

• Result:

The forward characteristics of a light emitting diode are obtained and the graph was plotted.

Experiment-5:

Title: Half Wave rectifier with and without diode.

Aim: To observe output waveforms and to find ripple factor of a half wave rectifier with and without filter.

• Apparatus:

- 0-12v stepdown transformer
- 1N407 diode
- multimeter
- 1000 Ω resistor
- 1000 μ F 125 V capacitor
- Bread-board
- Wires.

• Circuit Diagram:

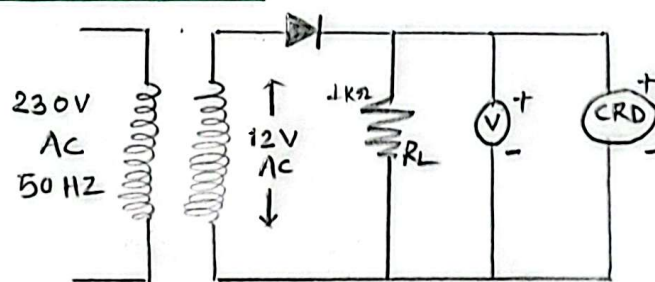


fig: Half Wave rectifier without filter.

• Table:

V_{AC}	V_{DC}	$R.F = \frac{V_{AC}}{V_{DC}}$
5.5	4.5	1.21

• Circuit Diagram:

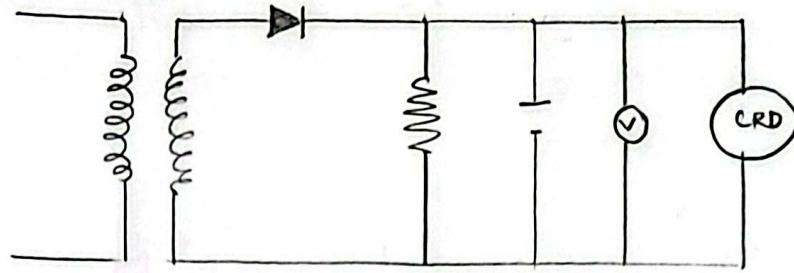


fig: Half Wave rectifier with filter


• Table:

V_{AC}	V_{DC}	$R.F = \frac{V_{AC}}{V_{DC}}$
0.0939	7.32	0.0128

• Procedure:

- Connection are made as per the circuit diagram
- Observe the CRO waveform and note down V_{DC} , V_{RMS} and other parameter.
- Add a 25 VOLT 1000MF capacitors filter.
- Again tabulate data from the CRO and DMM.

• Model graph:

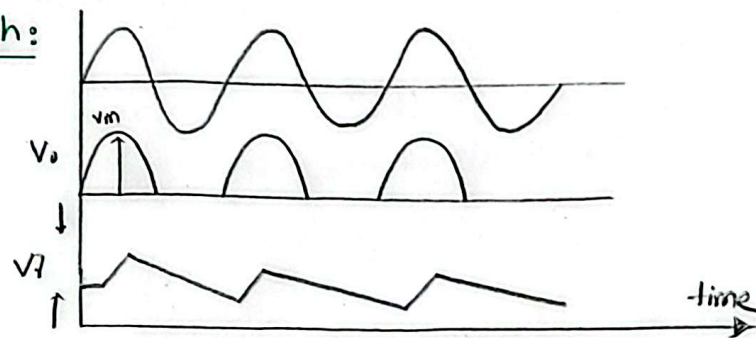

• Calculation:

• Without filter:

$$\begin{aligned}
 \sim V_{DC} &= V_m / \pi \\
 \sim V_{RMS} &= V_m / 2 \\
 \sim V_{r(RMS)} &= \sqrt{V_{RMS}^2 - V_{DC}^2} \\
 \sim \text{Ripple factor} &= V_{r(RMS)} / V_{DC}
 \end{aligned}$$

• With filter:

$$\begin{aligned}
 \sim V_{DC} &= V_m - V_r / 2 \\
 \sim V_{r(RMS)} &= V_r / 2\sqrt{3} \\
 \sim \text{Ripple factor} &= V_{r(RMS)} / V_{DC}
 \end{aligned}$$

• Precautions:

- Connection must be made carefully to avoid short circuit.
- Readings must be taken without parallel or error.

• Result:

- Ripple factor of Half wave rectifier Without filter:
- Ripple factor of Half wave rectifier With filter:

Experiment: 6:

• Title: Full wave rectifier With and without filter.

• AIM: To observe the output waveform and to find ripple factor of the center tapped full wave rectifier.

• Apparatus:

- i) Step down transformer ii) 1N4007 diodes-2 iii) Resistor 1000Ω
- iv) $1000\mu\text{F}/25\text{V}$ Capacitor v) Voltmeter (0-20V) vi) Bread board
- vii) Connecting wires.

• Circuit Diagram:

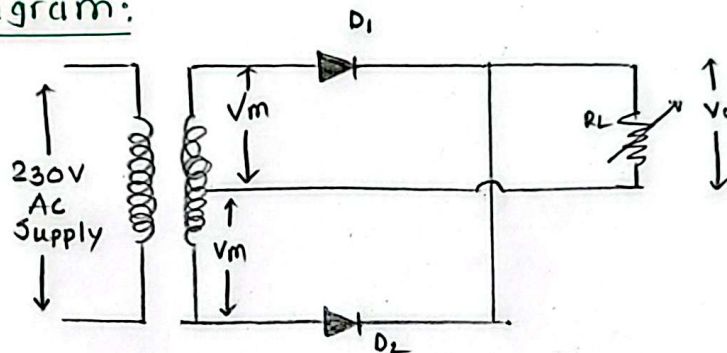


fig: Full Wave rectifier without filter.

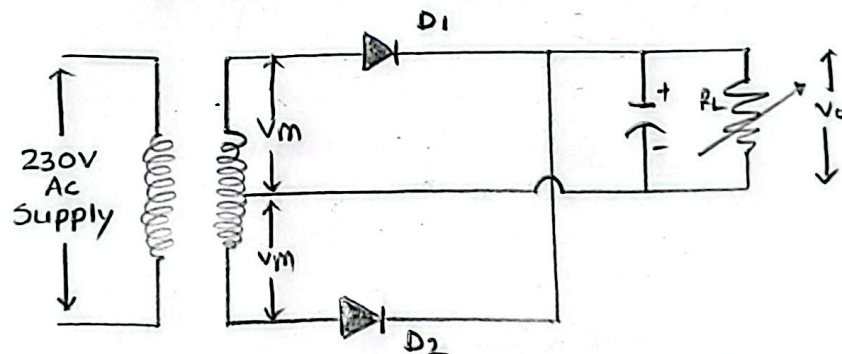



fig: Full wave rectifier with filter.

• Tabular form:

VAC	VDC	R.F. = V_{AC}/V_{DC}

VAC	VDC	R.F. = $\frac{V_{AC}}{V_{DC}}$

• Model graph:

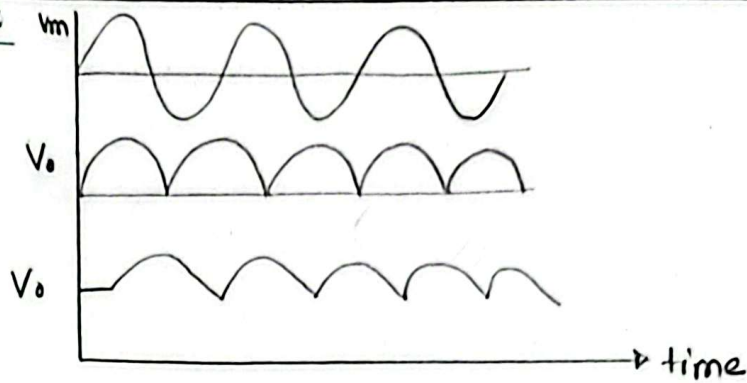

• Procedure:

- Connections are made as per the circuit diagram.
- Observe the output waveform on CRO. Note down the peak Voltage value V_m .
- Using DMM/multimeter down to the AC and DC voltage.
- Calculate V_{dc} , V_{rms} and Ripple factor.
- Connect a shunt capacitor and repeat the above process.
- plot the graphs.

• Calculations:

• Without filter:

- ✓ $V_{dc} = 2V_m/\pi$
- ✓ $V_{rms} = V_m/\sqrt{2}$
- ✓ $V_r(rms) = \sqrt{V_{rms}^2 - V_{dc}^2}$
- ✓ $R.F = (V_r)_{rms}/V_{dc}$

• With filter:

- ✓ $V_{dc} = V_m - V_r/2$
- ✓ $(V_r)_{rms} = V_r/2\sqrt{3}$
- ✓ $R.F = (V_r)_{rms}/V_{dc}$

• Precautions:

- Avoid loose and wrong connections.
- Avoid parallax error.

• Result:

- R.F of full wave rectifier with out filter =
- R.F of full wave rectifier with filter =