



DEPARTMENT OF COMPUTER SCIENCE & ENGINEERING
UNIVERSITY OF BARISAL

Final Examination

Course Title: Digital Logic Design

Course Code: CSE-2103

2nd Year 1st Semester

Session: 2020-21 (Admission Session 2019-20)

Time: 3 hour

Marks: 60

Answer any five Questions from the followings.

1. a) Implement the Boolean function


[3]

$$F = \bar{x}y + x'y' + y'z$$

- With AND, OR, and inverter gates,
- With NOR and inverter gates,
- With NAND and inverter gates.

- b) Show that a positive logic NAND gate is a negative logic NOR gate and vice versa. [3]

 - c) Write Boolean expressions and construct the truth tables describing the outputs of the circuits described by the following logic diagrams: [6]



2. a) Express the following function as a sum of minterms and as a product of maxterms: [2]

$$F(A, B, C, D) = B'D + A'D + BD$$

- b) Simplify the following Boolean functions, using Karnaugh maps: [6]

$$F(w, x, y, z) = \sum (2, 3, 12, 13, 14, 15)$$

$$F(A, B, C, D) = \sum (0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$$

- c) Implement the following Boolean function F, together with the don't-care conditions d, using no more than two NOR gates: [4]

$$F(A, B, C, D) = \sum (2, 4, 6, 10, 12)$$

$$d(A, B, C, D) = \sum (0, 8, 9, 13)$$

Assume that both the normal and complement inputs are available.

3. a) Explain how a NAND/NOR latch store a bit. Mention their limitations. [3]
 b) What is the limitation of S-R flip-flop? Explain how the limitation can be resolved. [4]
 c) Define race-around condition in J-K flip-flop. How can you overcome the problem? Explain with an appropriate figure and waveforms. [5]
4. a) What is the limitation of a parallel adder? Using 74LS83 ICs, draw a 16 bit parallel Adder. [3]
 b) Explain how 2's complement system can facilitate arithmetic operations in digital computing. [3]
 c) Draw a parallel adder/subtractor using 2's-complement system and explain its operations. [6]
5. a) Draw a Mod-14 and a Decade ripple counter with their state transition diagram. [4]
 b) Show how to wire the 74293 IC as a MOD-6 counter. [2]
 c) Explain the operation of a Synchronous up/down MOD-8 counter with an appropriate diagram. [6]
6. a) Write short notes on the followings: [5]
 I) Fan-Out
 II) Noise Immunity
 III) Propagation delay
 IV) Characteristics of TTL logic gate.
 b) Design and explain the working principle of a TTL NOR gate. [5]
 c) A certain TTL IC output is rated at $I_{OH}(\text{max}) = 800 \mu\text{A}$ and $I_{OL} = 48 \text{ mA}$. Express the IC's fan-out in terms of unit loads. [consider $1 \text{ UL} = 40 \mu\text{A}$ in the HIGH state and 1.6 mA in the LOW state] [2]
7. a) Design a 1 of 8 decoder using logic gates. [4]
 b) Use 74LS138 ICs to design a 1 of 32 decoder. [5]
 c) Draw the internal diagram of a 8:1 encoder. [3]
8. a) What is Multiplexer? Design an 8-input MUX and explain its operation. [4]
 b) How can you use a 74138 IC as a DEMUX? Explain with diagram. [4]
 c) Draw the logic diagram for the 7442 BCD to decimal decoder. [4]